

Moore FSM: (6 states)

S0: Initial State (Output = 0)


S1: The last bit received = 1 (Output = 0)

S2: The last two bits received, 10, (Output = 0)

S3: The FSM just detected '101' sequence (Output = 1)

S4: The sequence in 4 bit window is 1011, (Output = 1)

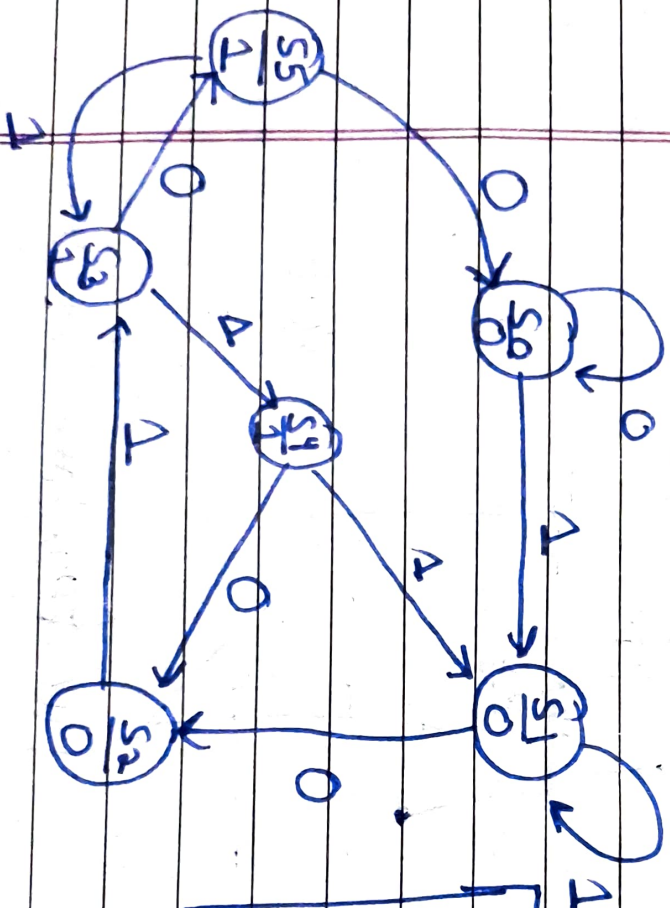S5: The sequence in 4 bit window is 1010, (Output = 1)



Moore
State
Diagram